Jameco Page number 140610

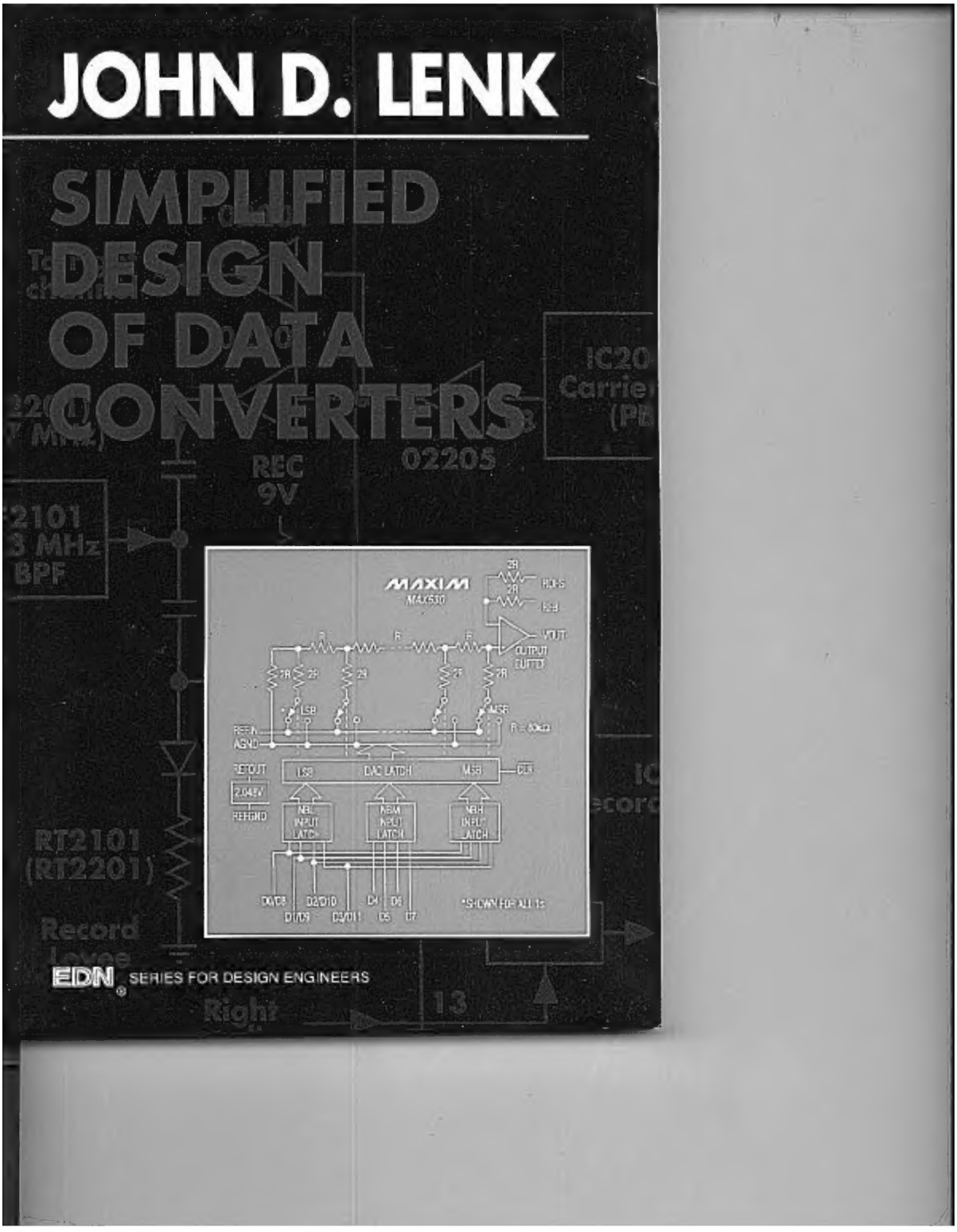

Jameco Page number 140610

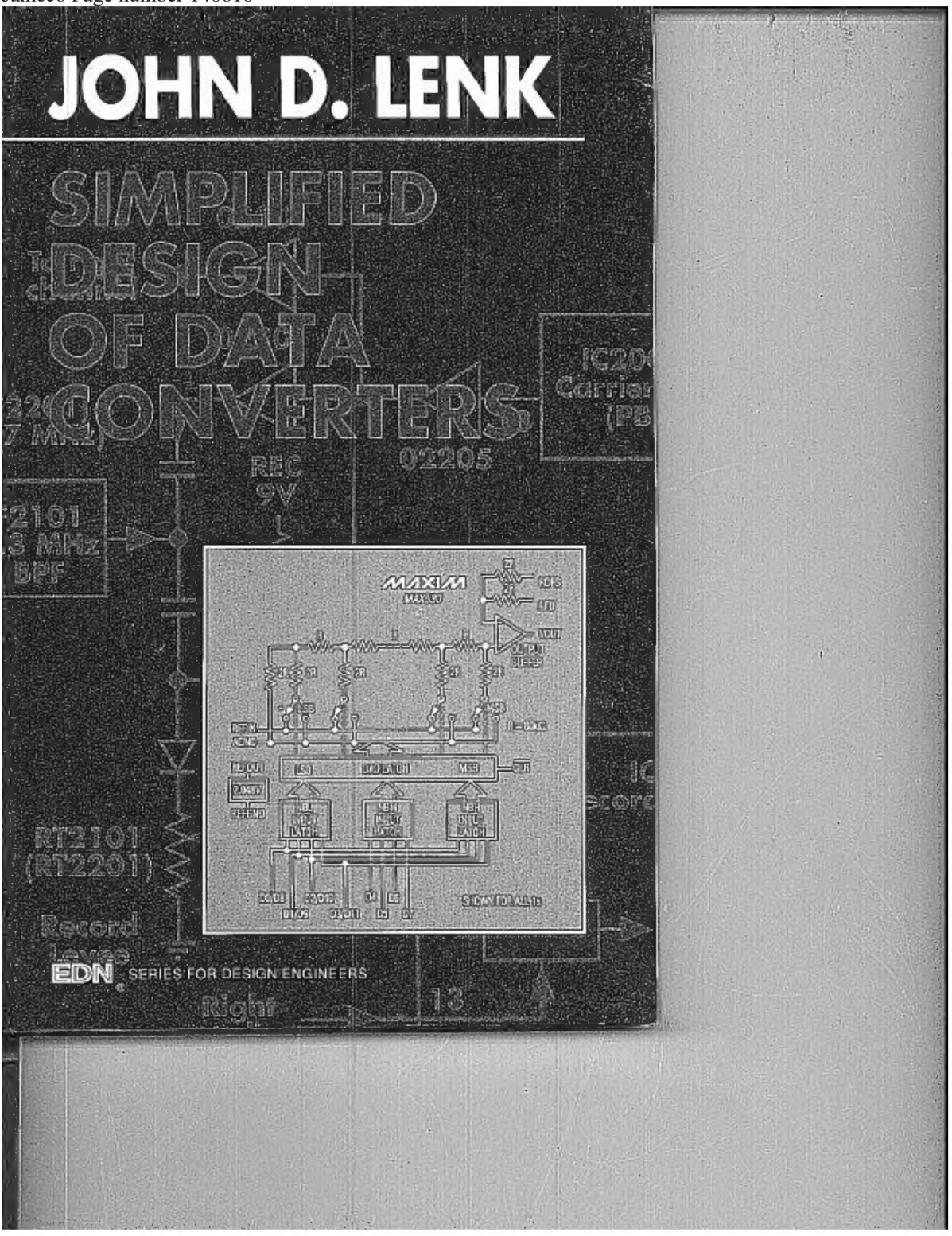

Jameco Page number 140610

Contents

Preface xi

Acknowledgments xiii

1 Data Converter Basics 1

1.1 Basic Data Conversion Techniques 1
1.2 Typical DAC IC 8
1.3 Typical ADC IC 18
1.4 Basic ADC/DAC Testing and Troubleshooting 29

2 Data-Converter Terms and Design Characteristics 39

2.1 Resolution and Accuracy 39
2.2 Linearity 40
2.3 Data Converter Errors 42
2.4 Differential Nonlinearity 45
2.5 Monotonicity 46
2.6 Settling Time and Slew Rate 47
2.7 Conversion Rate 47
2.8 Temperature Coefficient and Long-Term Drift 47
2.9 Overshoot and Glitches 48
2.10 Power Supply Rejection 49
2.11 Input Impedance and Output Drive 49
2.12 Clock Rate 49
2.13 Data-Converter Codes 49

3 Practical Design Considerations 53

3.1 Digital Control Signals 53
3.2 Voltage References 54
3.3 Multichannel Conversion 56
3.4 Track and Hold 58

3.5 Interfacing 58
3.6 Conversion Speed 61
3.7 AC Signal Processing 62
3.8 Noise Problems 62
3.9 Practical Layout 63

4 Simplified Design with a Typical ADC 65

4.1 General Description of ADC 65
4.2 Data-Converter Operation 65
4.3 Serial Interface Considerations 70
4.4 Dynamic Performance Characteristics and Testing 75
4.5 Application Data 78

5 Simplified Design with a Flash ADC 83

5.1 General Description of ADC 83
5.2 Data-Converter Operation 83
5.3 Power Requirements 85
5.4 Reference Voltage Requirements 85
5.5 Output Coding Control 88
5.6 Initiating a Conversion 89
5.7 Analog Inputs 89
5.8 Digital Outputs 89
5.9 Calibration 89
5.10 Typical Video Interface 91

6 Simplified Design with Serial-Interface DAC 93

6.1 General Description of DAC 93
6.2 Data-Converter Operation 94
6.3 Reference Inputs versus DAC Output Range 96
6.4 Output Buffer Amplifiers (DAC A/DAC B) 96
6.5 Unbuffered Output (DAC C) 97
6.6 Shutdown Mode 97
6.7 Reset 97
6.8 Serial Interface 97
6.9 Data Format and Control Codes 98
6.10 Digital Inputs 99
6.11 Digital Output 99
6.12 Microprocessor Interfacing 99
6.13 Applications Data 102

7 Simplified Design with Parallel-Input DAC 107

7.1 General Description of DAC 107
7.2 Data-Converter Operation 107

Jameco Page number 140610

7.3 R-2R Ladder 108
7.4 Internal Reference 110
7.5 Internal Reference Noise 110
7.6 Output Buffer-Amplifier 110
7.7 External Reference 111
7.8 Reset Functions 112
7.9 Shutdown Mode 112
7.10 Parallel Logic Interface 113
7.11 4-Bit Microprocessor Interface 116
7.12 8-Bit or 16-Bit Microprocessor Interface 116
7.13 Unipolar Operation 117
7.14 Bipolar Operation 119
7.15 Four-Quadrant Multiplication 120
7.16 Single-Supply Problems 120
7.17 Bypasses, Grounds, and PC-Board Layout 121
7.18 Digital and Analog Feedthrough 121

8 Simplified Design Approaches 123

8.1 References for ADCs and DACs 123
8.2 Unusual ADC Applications 128
8.3 Data Acquisition with ADCs 131
8.4 Circuit Applications with Multiplying DACs 160
8.5 Some Classic CMOS DAC Applications 166

9 Low-Power Data-Acquisition System 177

9.1 General Description of ADC 177
9.2 Data-Converter Operation 178
9.3 Applications Information 189

10 Single-Chip Digital Multimeter 203

10.1 System Considerations 203
10.2 Digital Interface 212
10.3 Component Selection 218
10.4 Conversion Method 220
10.5 Application Notes 224
10.6 Software Notes 226
10.7 Using the IC in Data-Acquisition Systems 228

For Further Information 233

Index 236